

## Evaluation Board Report

### 12V 1.8W ACDC power supply

Design Specs	Value	Unit
Input Voltage	85-265	VAC
Output Voltage	12	VDC
Output Current	0.15	A
Isolation	No	
MPS IC	MP156GJ	
Application	Home Appliance, white goods, consumer electronics Industrial Controls Standby Power	

Document Number	EBXXX
Author	Application Engineering Department
Date	Nov, 2014
Revision	1.0

### Design Summary

EV156-J-00A evaluation board provides a reference design for a universal offline power supply with 12V, 0.15A output. It contains the complete specification of the power supply, a detailed circuit diagram, the entire bill of materials required to build the power supply, drawing of the power inductors and transformers, and test data of the most important performance.

## DESCRIPTION

MP156 is a primary-side regulator that provides accurate constant voltage (CV) regulation without opto-coupler, support buck, buck-boost, or flyback topologies. It has an integrated 500V MOSFET to simplify the structure and reduce costs. These features make it a competitive candidate for off-line low power applications, such as home appliances and standby power.

MP156 is a green-mode-operation regulator. Both its the peak current and the switching frequency decrease as the load decreases to provide excellent efficiency at light load, thus improving the overall average efficiency.

MP156 features various protections, including thermal shutdown (TSD), VCC under-voltage lockout (UVLO), overload protection (OLP), short-circuit protection (SCP), and open loop protection.

MP156 is available in the TSOT23-5 and SOIC8 package.

## FEATURES


- Primary-Side Constant Voltage (CV) Control, Supporting buck, Buck-Boost and Flyback Topologies
- Integrated 500V/20Ω MOSFET
- <30mW No-Load Power Consumption
- Up to 3W Output Power
- Maximum DCM Output Current Less than 130mA
- Maximum CCM Output Current Less than 220mA
- Low VCC Operating Current
- Frequency Foldback
- Limited Maximum Frequency
- Peak-Current Compression
- Internal High-Voltage Current Source
- Internal 350ns Leading-Edge Blanking
- Thermal Shutdown (Auto Restart)
- VCC Under Voltage Lockout with Hysteresis
- Timer Based Over-Load Protection.
- Short-Circuit Protection
- Open-Loop Protection

## EV156-J-00A EVALUATION BOARD



( L x W x H ) 3.4cm x 2.2cm x 1.6cm

Board Number	MPS IC Number
EV156-J-00A	MP156GJ

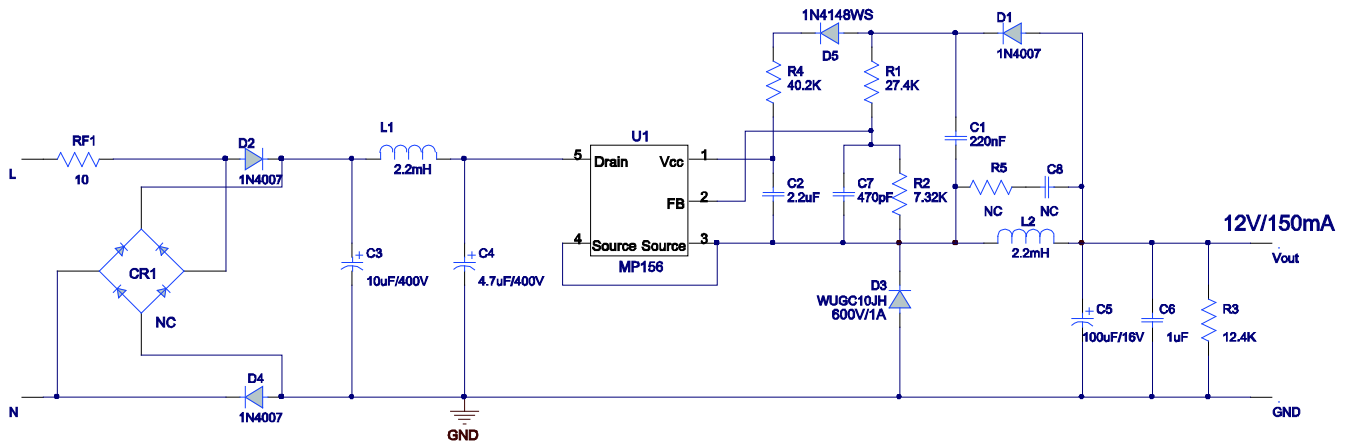**EVALUATION BOARD SCHEMATIC**


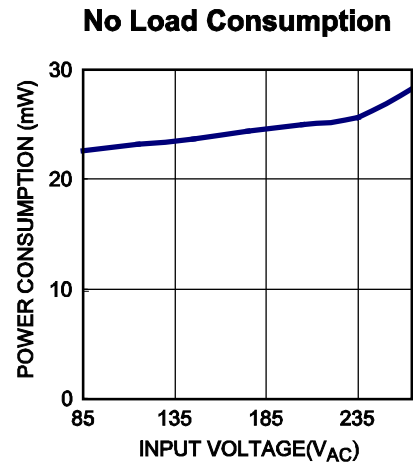
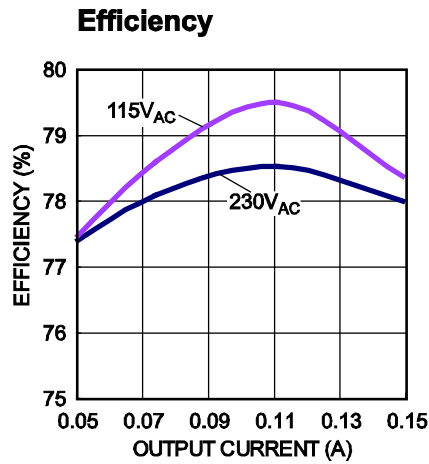
**EV156-J-00A BILL OF MATERIALS**

Qty	RefDes	Value	Description	Package	Manufacture	Manufacture_PN
1	C1	220nF	Ceramic Capacitor;16V;X7R ;0603;	0603	muRata	GRM188R71C224KA01D
1	C2	2.2uF	Ceramic Capacitor;10V;X7R ;0603	0603	muRata	GRM188R71A225KE15D
1	C3	10uF/400V	Electrolytic Capacitor;400V;20 %	DIP	Any	Any
1	C4	4.7uF/400V	Electrolytic Capacitor;400V;Ele ctrolytic;DIP	DIP	Jianghai	CD263-400V4.7
1	C5	100uF/16V	Electrolytic Capacitor;16V;Elec trolytic;DIP	DIP	Jianghai	CD11C-16V100
1	C6	1uF	Ceramic Capacitor;50V;X7R ;0805;	0805	muRata	GRM21BR71H105KA12L
1	C7	470pF	Ceramic Capacitor;50V;CO G	0603	TDK	C1608COG1H471J
3	D1, D2, D4	1N4007	Diode;1000V;1A	DO-41	Diodes	1N4007
1	D3	WUGC10JH	Diode;600V;1A	SMA	ZOWIE	WUGC10JH
1	D5	1N4148WS	Diode;75V;0.15A;	SOD-323	Diodes	1N4148WS-7-F
1	L1	2.2mH	Inductor;2.2mH;11; 210mA	DIP	Würth	744741222
1	L2	2.2mH	Inductor;2.2mH;4.7 3;300mA	DIP	Würth	7447720222
1	R1	27.4K	Film Resistor;1%	0603	Yageo	RC0603FR-0727K4L
1	R2	7.32K	Film Resistor;1%	0603	Yageo	RC0603FR-077K32L
1	R3	12.4K	Film Resistor;1%;	0603	Yageo	RC0603FR-0712K4L
1	R4	40.2K	Film Resistor;1%;	0603	Yageo	RC0603FR-0740K2L
1	RF1	10	Fuse Resistor;5%;1W	DIP	Any	Any
1	U1	MP156GJ	Primary side regulator	TSOT23-5	MPS	MP156GJ

## EVB TEST RESULTS


Performance waveforms are tested on the evaluation board.

$V_{IN} = 85V$  to  $265V_{AC}$ ,  $V_{OUT} = 12V$ ,  $I_{OUT} = 150mA$ ,  $T_A = 25^{\circ}C$ , unless otherwise noted.




### Normal Operation

$V_{IN} = 115V_{AC}$ , Full Load

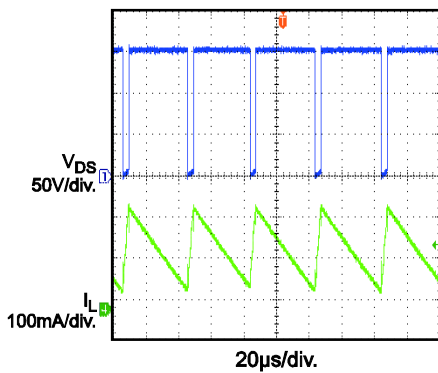


### Normal Operation

$V_{IN} = 230V_{AC}$ , Full Load

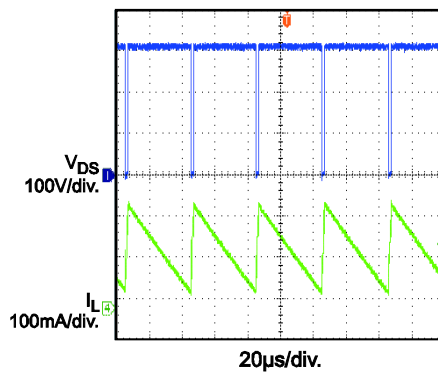


### Output Ripple

$V_{IN} = 115V_{AC}$ , No Load

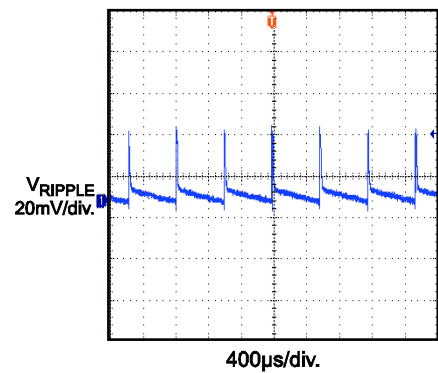


### Output Ripple

$V_{IN} = 115V_{AC}$ , Full Load

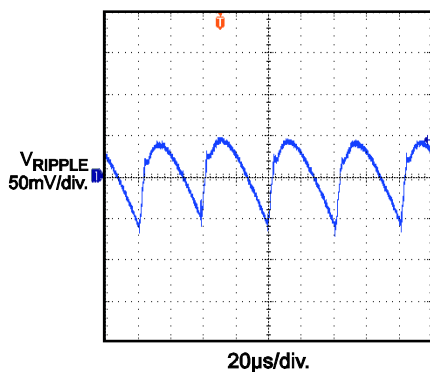


### Output Ripple

$V_{IN} = 230V_{AC}$ , No Load

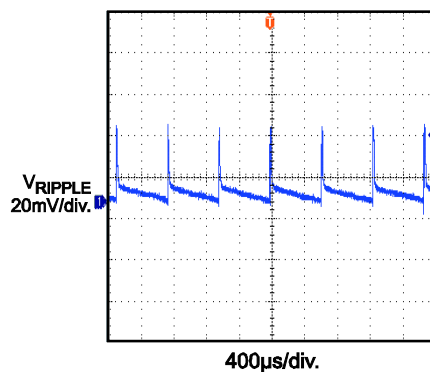

### Output Ripple










$V_{IN} = 230V_{AC}$ , Full Load

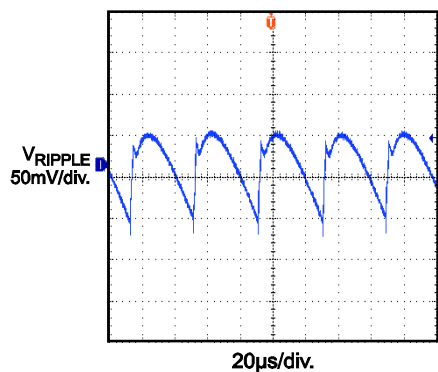

**EVB TEST RESULTS** *(continued)*









Performance waveforms are tested on the evaluation board.

 $V_{IN} = 85V$  to  $265V_{AC}$ ,  $V_{OUT} = 12V$ ,  $I_{OUT} = 150mA$ ,  $T_A = 25^{\circ}C$ , unless otherwise noted.

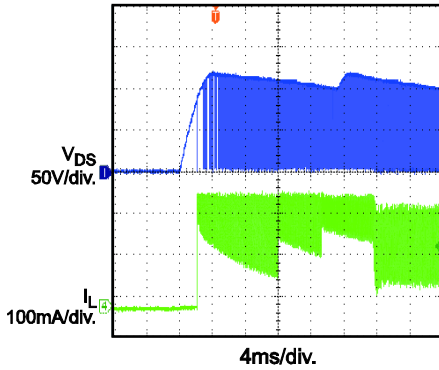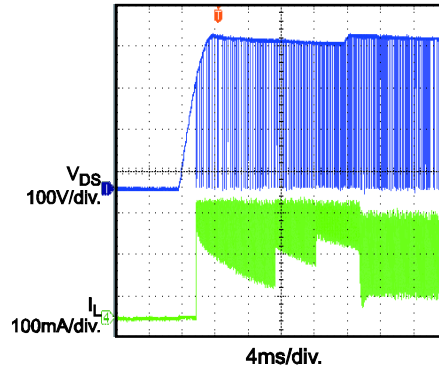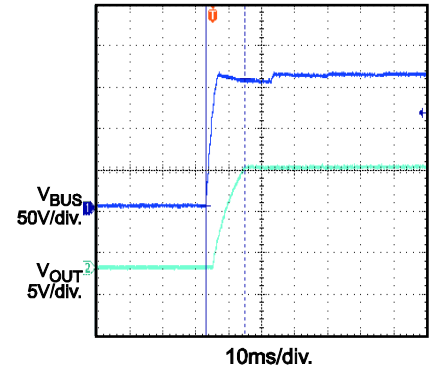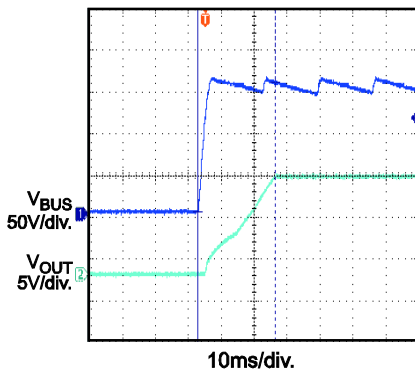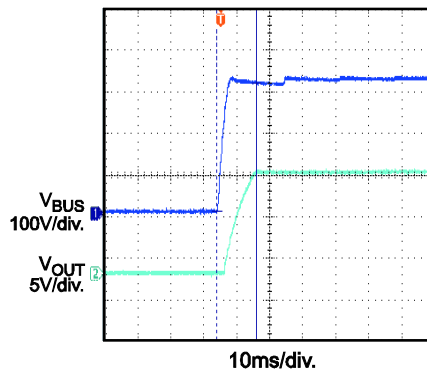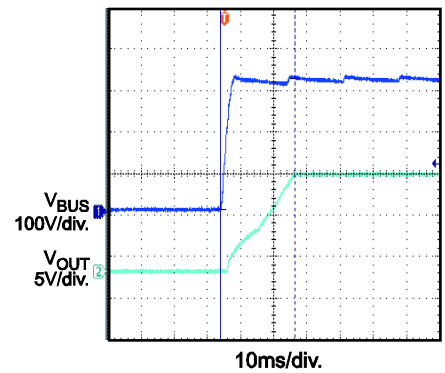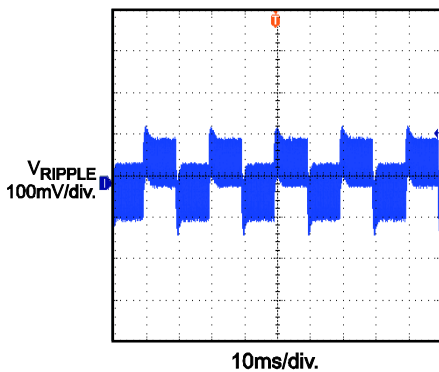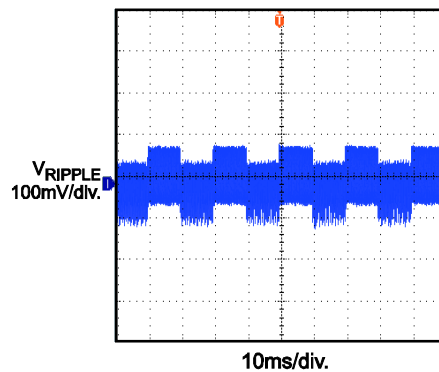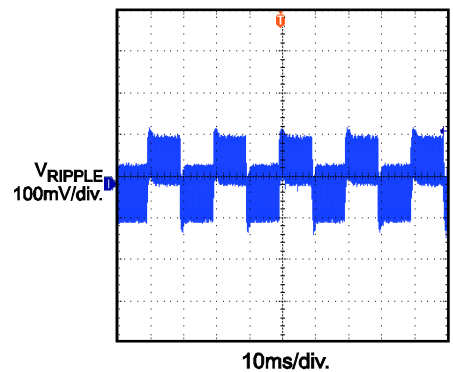**Soft Start**
 $V_{IN} = 85V_{AC}$ , Full Load

**Soft Start**
 $V_{IN} = 265V_{AC}$ , Full Load

**Turn-on Delay**
 $V_{IN} = 115V_{AC}$ , No Load

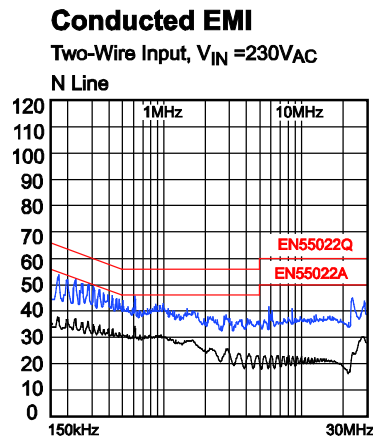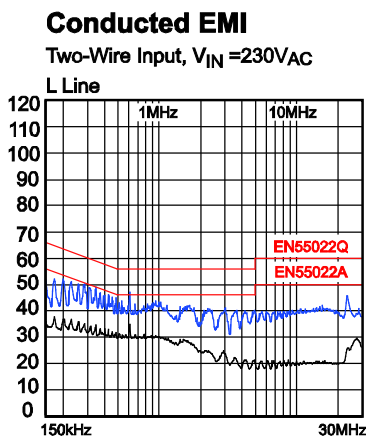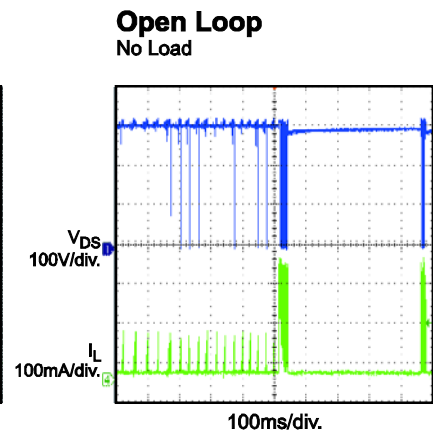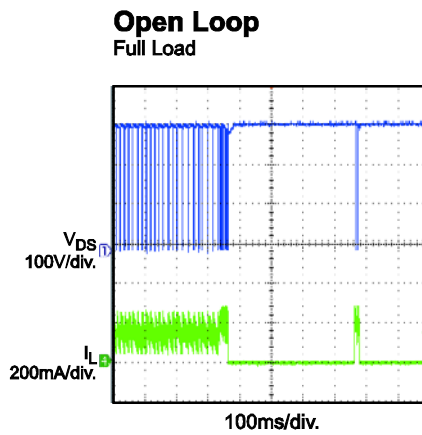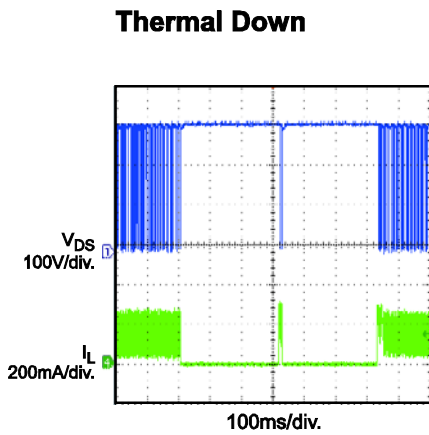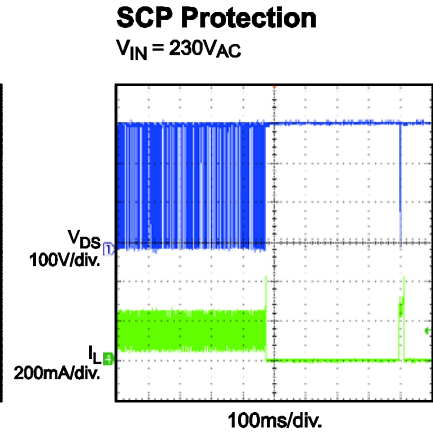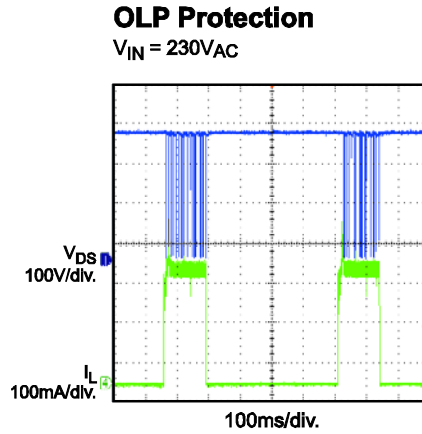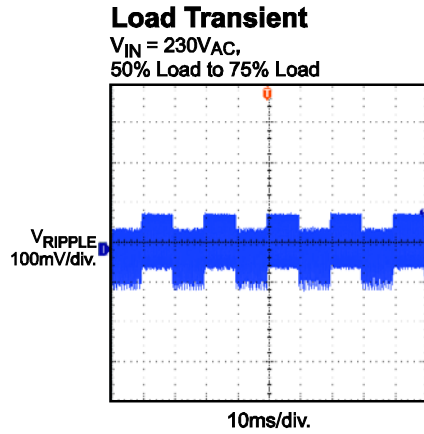**Turn-on Delay**
 $V_{IN} = 115V_{AC}$ , Full Load

**Turn-on Delay**
 $V_{IN} = 230V_{AC}$ , No Load

**Turn-on Delay**
 $V_{IN} = 230V_{AC}$ , Full Load

**Load Transient**
 $V_{IN} = 115V_{AC}$ ,  
25% Load to 50% Load

**Load Transient**
 $V_{IN} = 115V_{AC}$ ,  
50% Load to 75% Load

**Load Transient**
 $V_{IN} = 230V_{AC}$ ,  
25% Load to 50% Load


**EVB TEST RESULTS** *(continued)*

Performance waveforms are tested on the evaluation board.

 $V_{IN} = 85V$  to  $265V_{AC}$ ,  $V_{OUT} = 12V$ ,  $I_{OUT} = 150mA$ ,  $T_A = 25^{\circ}C$ , unless otherwise noted.


## SURGE PERFORMANCE

With the input capacitors C3 (10 $\mu$ F) and C4 (4.7 $\mu$ F), the board can pass 1kV surge test. Table 1 shows the capacitance required under normal condition for different surge voltage.

Table 1: Recommended Capacitor Values

Surge Voltage	500V	1000V	2000V
C3	1 $\mu$ F	10 $\mu$ F	22 $\mu$ F
C4	1 $\mu$ F	4.7 $\mu$ F	10 $\mu$ F

## PRINTED CIRCUIT BOARD LAYOUT

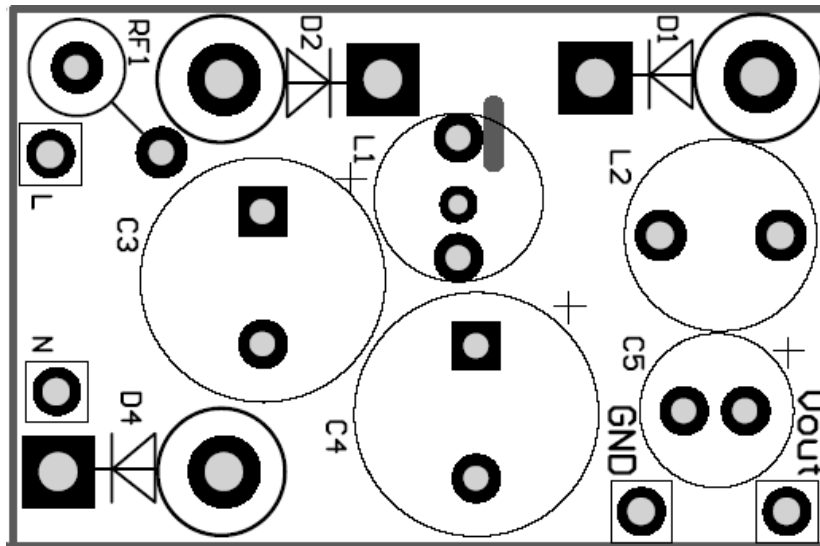


Figure 1 — Top Silk Layer

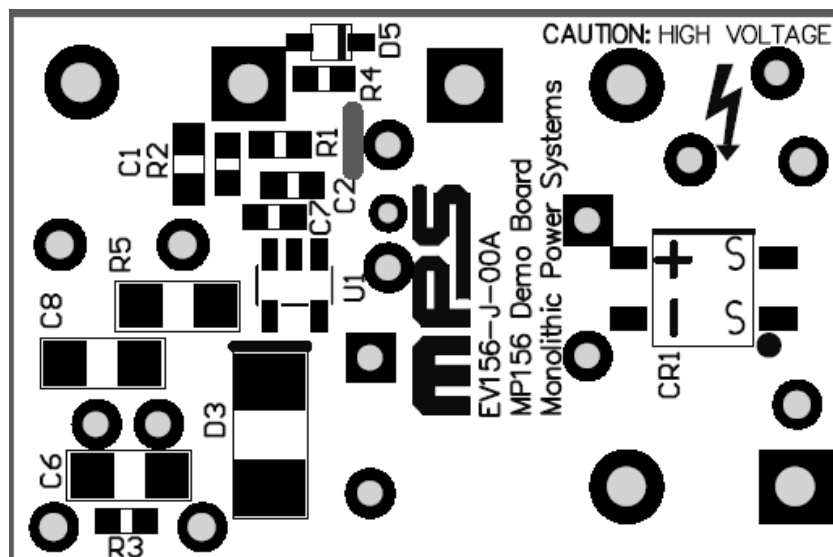


Figure 2 — Bottom Silk Layer



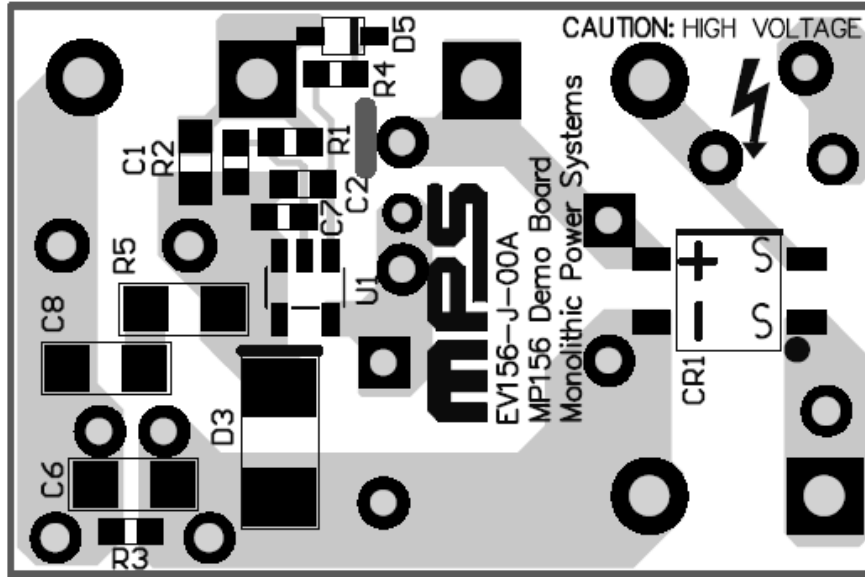


Figure 3 — Bottom Layer

## QUICK START GUIDE

1. Preset Power Supply to  $85V \leq V_{IN} \leq 265V$ .
2. Turn Power Supply off.
3. Connect the Line and Neutral terminals of the power supply output to L and N port.
4. Connect the positive terminal of the load to  $V_{OUT}$  port, and connect the negative terminal of the load to GND port.
5. Turn Power Supply on after making connections.

## Contact Information

To request this evaluation board, please refer to your local sales offices which can be found from:

<http://www.monolithicpower.com/Company/Contact-Us>

## Disclaimer

Monolithic Power Systems (MPS) reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. MPS makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

MPS cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a MPS product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage (“Critical Applications”).

**MPS PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICALAPPLICATIONS.**

Inclusion of MPS products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to MPS.

MPS semiconductors are typically used in power supplies in which high voltages are present during operation. High voltage safety precautions should be observed in design and operation to minimize the chance of injury.

**NOTICE:** The information in this document is subject to change without notice. Please contact MPS for current specifications. Users should warrant and guarantee that third party Intellectual Property rights are not infringed upon when integrating MPS products into any application. MPS will not assume any legal responsibility for any said applications.